



## L7: Memory Basics and Timing



**Acknowledgement: Nathan Ickes**

*Some slides are derived from slides used in past terms of 6.111*

L7 6.111 Fall 2003 – Introductory Digital Systems Laboratory

1



## Memory Classification & Metrics



Read-Write Memory		Non-Volatile Read-Write Memory	Read-Only Memory
Random Access	Non-Random Access	EPROM E <sup>2</sup> PROM FLASH	Mask-Programmed
SRAM DRAM	FIFO LIFO		

### Key Design Metrics:


1. Memory Density (number of bits/ $\mu\text{m}^2$ ) and Size
2. Access Time (time to read or write) and Throughput
3. Power Dissipation

L7 6.111 Fall 2003 – Introductory Digital Systems Laboratory - Copyright © 2003 by MIT

2




## Memory Array Architecture

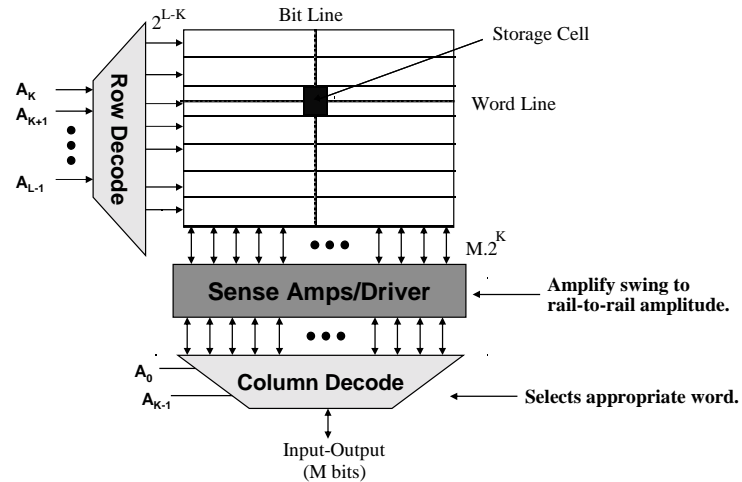


## Latch- and Register-Based Memory



### Positive Latch Negative Latch

 

### Register Memory

 


- Works fine for small memory blocks (e.g., small register files).
- Inefficient in area for large memories
- Density is the key metric in large memory circuits.

*How do we minimize cell size?*



## Static RAM (SRAM) Cell (The 6-T Cell)

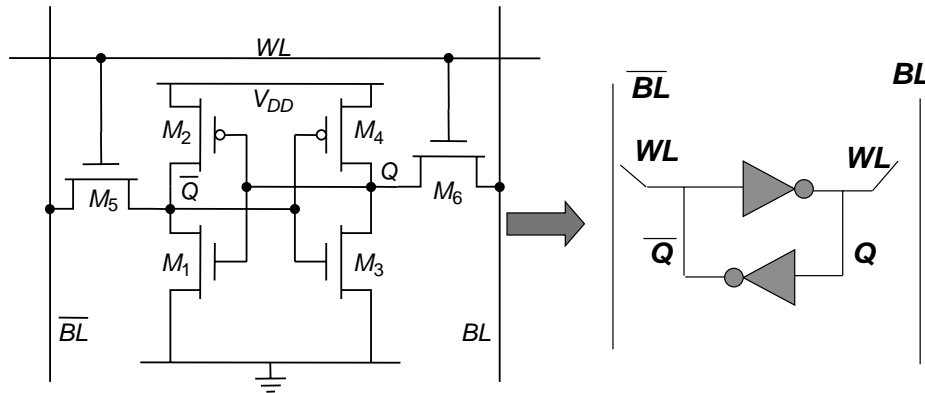


- State held by cross-coupled inverters (M1-M4).
- Retains state as long as power supply turned on
- Feedback must be overdriven to write into the memory.

L7 6.111 Fall 2003 – Introductory Digital Systems Laboratory - Copyright © 2003 by MIT

5



## Dynamic RAM (DRAM) Cell

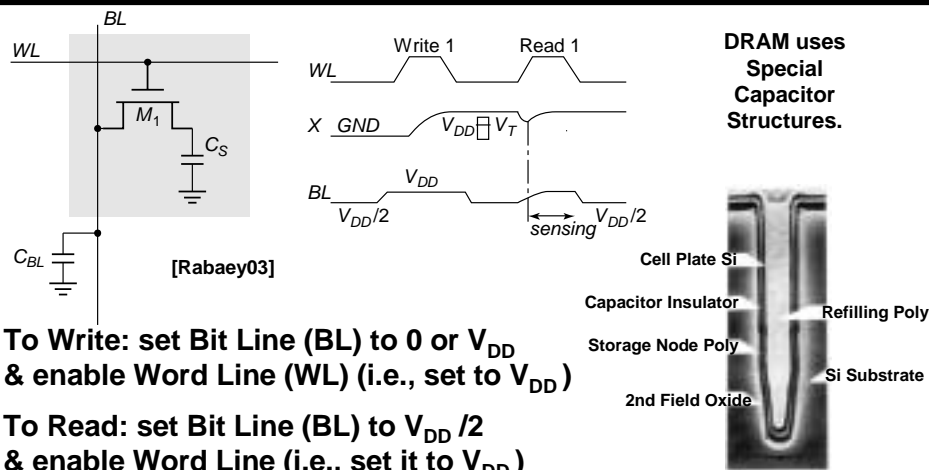

**To Write:** set Bit Line (BL) to 0 or  $V_{DD}$  & enable Word Line (WL) (i.e., set to  $V_{DD}$ )

**To Read:** set Bit Line (BL) to  $V_{DD}/2$  & enable Word Line (i.e., set it to  $V_{DD}$ )


- DRAM relies on charge stored in a capacitor to hold state.
- Found in all high-density memories (one bit/transistor)
- Must be “refreshed” or state will be lost – high overhead

L7 6.111 Fall 2003 – Introductory Digital Systems Laboratory - Copyright © 2003 by MIT

6



 
## EPROM Cell – The Floating Gate Transistor



### EPROM Cell

*Courtesy Intel*

 

**This non-volatile memory retains state when supply is turned off.**

L7 6.111 Fall 2003 – Introductory Digital Systems Laboratory - Copyright © 2003 by MIT

7



## EEPROM / FLASH





- Like EPROM, both EEPROM and FLASH technology use floating gate transistors.
  - The primary difference is that EEPROM and FLASH allow electrical erasing while EPROM is UV erasable.
- EPROM and FLASH use FAMOS (Floating gate Avalanche MOS) storage transistors.
  - The floating gate of the FAMOS transistors gets its electrons by avalanche (hot electron) injection.
  - EPROM is erased by UV (~35 minutes).
  - FLASH is erased by tunneling.
- EEPROM uses FLOTOX (Floating gate Tunnel Oxide storage transistors).
  - The floating gate of an EEPROM gets its electrons by Fowler-Nordheim tunneling.
- EEPROM and FLASH are erased by sections.
  - not individual bits so they are not like SRAMS

L7 6.111 Fall 2003 – Introductory Digital Systems Laboratory - Copyright © 2003 by MIT

8



## Density/Size Memory Trends

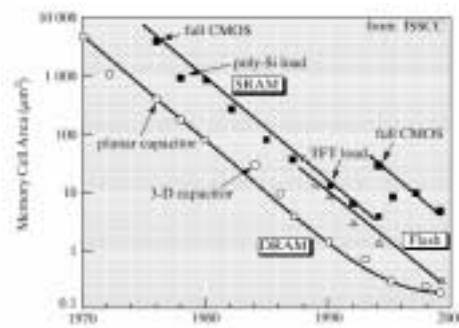 

From [Itoh01]



## Key Messages on Memory Devices



- **SRAM vs. DRAM**
  - SRAM holds state as long as power supply is turned on. DRAM must be “refreshed” – results in more complicated control.
  - DRAM has much higher density, but requires special capacitor technology.
  - FPGA usually implemented in a standard digital process technology and uses SRAM technology
- **Non-Volatile Memory**
  - Fast Read, but very slow write (EPROM must be removed from the system for programming!)
  - Holds state even if the power supply is turned off
- **Memory Internals**
  - Has quite a bit of analog circuits internally
  - Pay particular attention to noise and PC board integration.
- **Device details**
  - Don’t worry about them, wait until 6.012, 6.371 or 6.374.



## MCM6264C 8k x 8 Static RAM



- Same (bidirectional) data bus used for reading and writing

- Chip Enables ( $\overline{E1}$  and  $E2$ )


- $\overline{E1}$  must be low and  $E2$  must be high to enable the chip.

- Write Enable ( $\overline{W}$ )

- When low (and chip is enabled), the values on the data bus are written to the location selected by the address bus.

- Output Enable ( $\overline{G}$ )

 
- When low (and chip is enabled), the data bus is driven with the value of the selected memory location.



NC	1	28	V <sub>CC</sub>
A12	2	27	W
A11	3	26	E2
A10	4	25	A0
A9	5	24	A1
A8	6	23	A11
A7	7	22	E1
A6	8	21	A10
A5	9	20	V <sub>CC</sub>
A4	10	19	DQ27
DQ15	11	18	DQ26
DQ14	12	17	DQ25
DQ13	13	16	DQ24
DQ12	14	15	DQ23




## Inside the '6264C

 




## Reading From SRAM

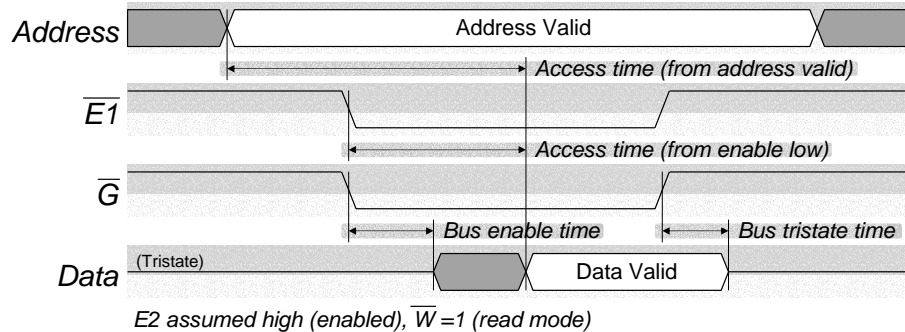

- Read cycle begins when all enable signals ( $\overline{E1}$ ,  $E2$ ,  $\overline{G}$ ) are active.
- Data is valid after read access time.
  - Access time is indicated by full part number: *MCM6264CP-12* → 12ns.
- Data bus is tristated shortly after  $\overline{G}$  or  $\overline{E1}$  goes high.




## Address Controlled Reads

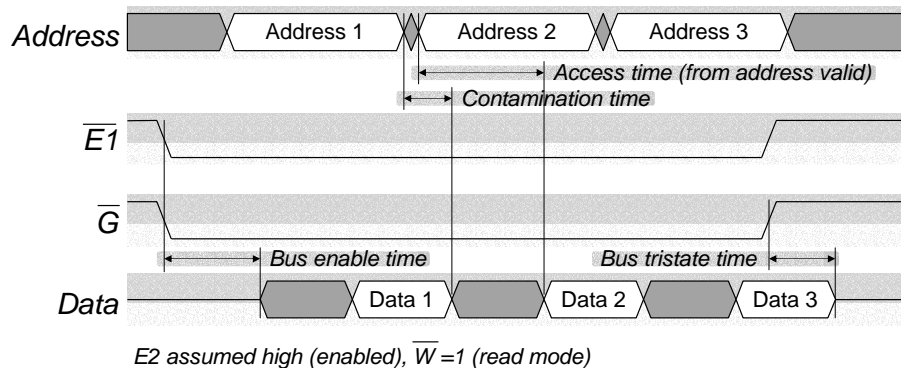

- Can perform multiple reads without disabling chip
- Data bus follows address bus, after some delay.



## Writing to SRAM

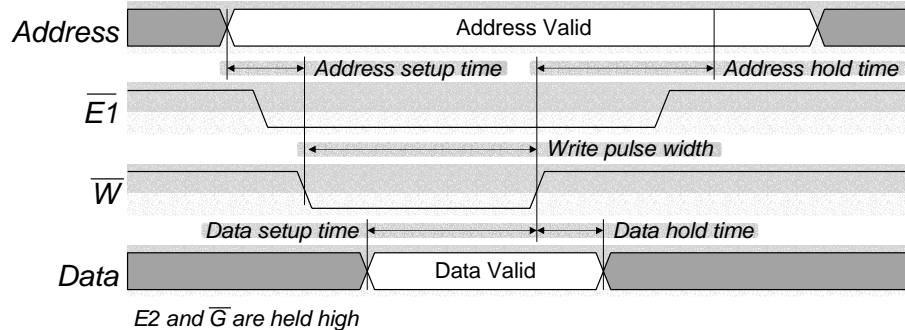

- Data latched when  $\overline{W}$  or  $\overline{E1}$  goes high (or E2 goes low)
  - Data must be stable at this time.
  - Address must be stable before  $\overline{W}$  goes low.
- Write waveforms are more important than read waveforms.
  - Glitches can cause writes to random addresses!

L7 6.111 Fall 2003 – Introductory Digital Systems Laboratory - Copyright © 2003 by MIT

15




## Flash and (E)EPROM



- Reading from flash or (E)EPROM is the same as reading from SRAM.
- $V_{pp}$ : input for programming voltage (12V)
  - EPROM:  $V_{pp}$  is supplied by programming machine.
  - Modern flash/EEPROM devices generate 12V using an on-chip charge pump.
- EPROM lacks a write enable.
  - Not in-system programmable (must use a special programming machine)
- For flash and EEPROM, write sequence is controlled by an internal FSM.
  - Writes to device are used to send signals to the FSM.
  - Although the same signals are used, one can't write to flash/EEPROM in the same manner as SRAM.

Flash/EEPROM block diagram

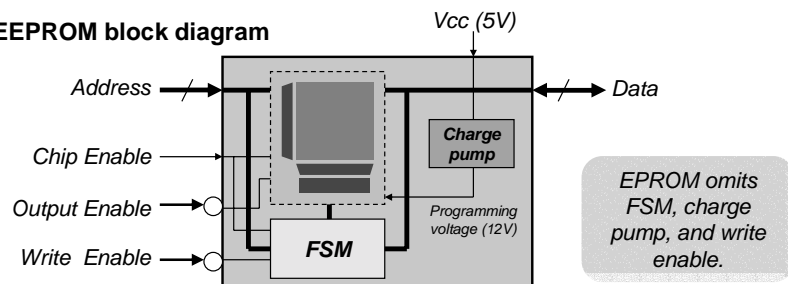


L7 6.111 Fall 2003 – Introductory Digital Systems Laboratory - Copyright © 2003 by MIT

16






## Sample Memory Interface Logic

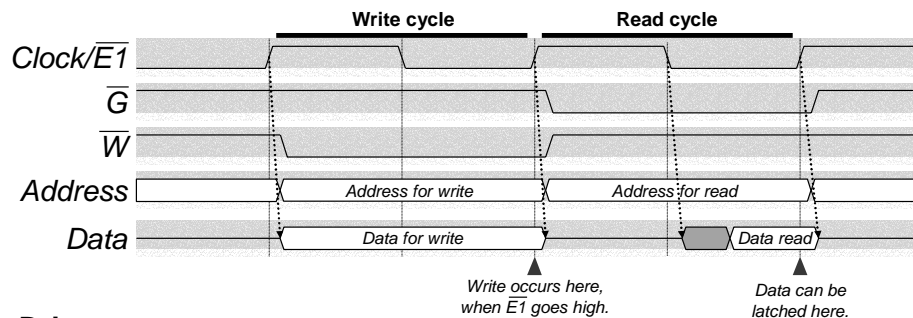
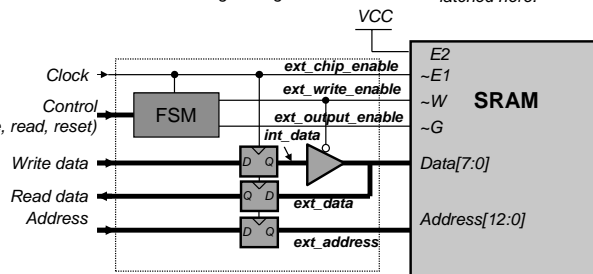
### ■ Drive memory enable with clock

- Ensures data and memory busses are stable for writes
- Minimum clock period is twice memory access time.



L7 6.111 Fall 2003 – Introductory Digital Systems Laboratory - Copyright © 2003 by MIT

17



## Toy Memory Interface in VHDL (I)



```

library ieee;
use ieee.std_logic_1164.all;

entity mem_int is
  port (clock : in std_logic;
        reset : in std_logic;
        write : in std_logic;
        read : in std_logic;
        address : in std_logic_vector(12 downto 0);
        write_data : in std_logic_vector(7 downto 0);
        read_data : out std_logic_vector(7 downto 0);
        ext_chip_enable : out std_logic;
        ext_write_enable : out std_logic;
        ext_output_enable : out std_logic;
        ext_address : out std_logic_vector(12 downto 0);
        ext_data : inout std_logic_vector(7 downto 0));
end mem_int;

architecture behavioral of mem_int is

  signal int_data : std_logic_vector(7 downto 0);

  (cont. on next viewgraph)

```

L7 6.111 Fall 2003 – Introductory Digital Systems Laboratory - Copyright © 2003 by MIT

18



## Toy Memory Interface in VHDL (II)



```

begin
  ext_chip_enable <= clock;
  ext_data <= int_data when ext_write_enable = '0' else (others => 'Z');

  process (clock, reset)
  begin
    if reset = '0' then
      ext_write_enable <= '1';
      ext_output_enable <= '1';
    elsif clock'event and clock = '1' then
      ext_address <= address;
      read_data <= ext_data;
      int_data <= write_data;
      if write = '1' then
        ext_write_enable <= '0';
      elsif read = '1' then
        ext_output_enable <= '0';
      else
        ext_write_enable <= '1';
        ext_output_enable <= '1';
      end if;
    end if;
  end process;

  end behavioral;



```


  
## Creating Larger Memories



- '138 is a 3-to-8 decoder.
  - Maps 16-bit address space to eight 13-bit segments
  - Upper 3 bits of address determine which chip is enabled.
- SRAM-like interface is often used for peripherals.
  - Referred to as “memory mapped peripherals”





## Testing Memories



- **Common device problems**
  - **Bad locations:** rare for individual locations to be bad
  - **Slow (out-of-spec) timings:** causes intermittent failures
  - **Catastrophic device failure:** e.g., ESD
  - **Missing wire-bonds/devices (!):** possible with automated assembly
  - **Transient failures:** Alpha particles, power supply glitch
- **Common circuit problems**
  - **Stuck-at-Faults:** a pin shorted to VDD or GND
  - **Open Circuit Fault:** connections unintentionally left out
  - **Open or shorted address wires:** causes data to be written to incorrect locations
  - **Open or shorted control wires:** generally renders memory completely inoperable



## Testing Memory



- **Since device problems generally affect the entire chip, almost any test will detect them.**
- **Writing (and reading back) many different data patterns can detect data bus problems.**
- **Writing unique data to every location and then reading it back can detect address bus problems.**



## Testing Memory




### ■ An idea that almost works

1. Write 0 to location 0.
2. Read location 0, compare value read with 0.
3. Write 1 to location 1.
4. Read location 1, compare value read with 1.
5. ...
 
### ■ What is the problem?

- Suppose the memory was missing (or output enable was disconnected)



**Data bus is undriven but wire capacitance briefly maintains the bus state: memory appears to be ok!**




## Testing Memory


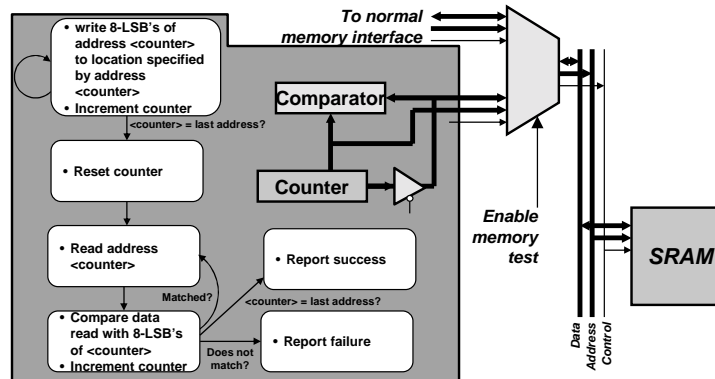
### ■ Write to all locations, then read back all locations.

- Separates read/write to the same location with reads/writes of different data to different locations
- (both data and address busses are changed between read and write to same location)

- Write 0 to address 0.
- Write 1 to address 1.
- ...
- Write  $(n \bmod 256)$  to address  $n$ .
- Read address 0, compare with 0.
- Read address 1, compare with 1.
- ...
- Read address  $n$ , compare with  $(n \bmod 256)$ .





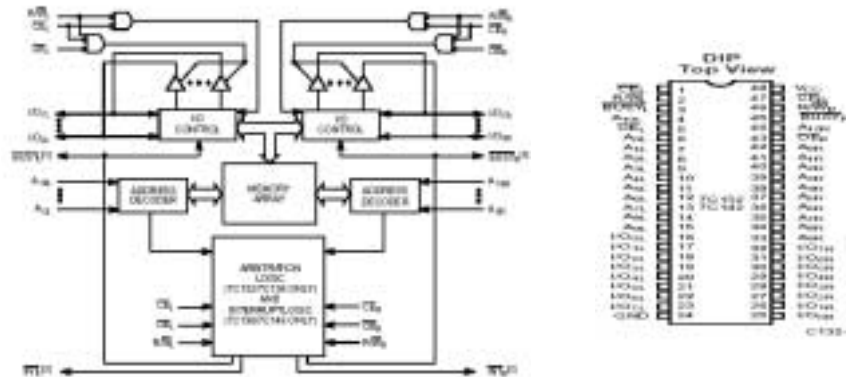
## Multi-Port Memories



- **Applications**
  - Register files, FIFO, buffer, etc.
- **Cypress CY7C132 2kx8 dual-port SRAM**
  - Two independent, asynchronous read/write ports
  - Can access two different memory locations simultaneously
  - Busy signal indicates if both ports attempt to access same location at the same time



L7 6.111 Fall 2003 – Introductory Digital Systems Laboratory - Copyright © 2003 by MIT

25




## Building a FIFO




- **Head pointer:** points to next available location for writing
- **Tail pointer:** points to next available location for reading
- If head and tail pointers are the same, FIFO is empty.
- If  $head+1 = tail$ , FIFO is full.
- Pointers wrap around when they reach the end of the memory.


Empty

 

After 4 writes and 2 reads

 

Full

 

L7 6.111 Fall 2003 – Introductory Digital Systems Laboratory - Copyright © 2003 by MIT

26



## Building a FIFO

